



■■■ Notes: I have tested the circuit above. ■■■

- I can't say if this sounds anything like an MS20, probably not, but it does sound pretty good.
- Signal greater than about +-2V overdrive the filter.
- The strings of diodes could be exchanged with LEDs.
- +7.5V came from an opamp. I tried using another inverter but it did not work as well. Try with some bypass caps. (I had none)
- Current source is linear. Try the expo source from the original.
- Filter self-oscillates easily, but does not produce a pure sinusoid.
- VC-resonance would be nice, but needs another OTA. I may try with cutoff dependent resonance, to allow super high res at low cutoff, without the whistle sound at high cutoff.

CMOSed Version of René Schmitz MS-20 Filter

Ryan Williams

Title:

Size: A4 Date: 19 nov 2005

KiCad E.D.A. EESchema (14-oct-2005)

Rev: 1/1
Sheet: 1/1